


STUDENT NAME.....Period.....Date:.....  
SPS22H: HONORS PHYSICS  
Dr. Majewski


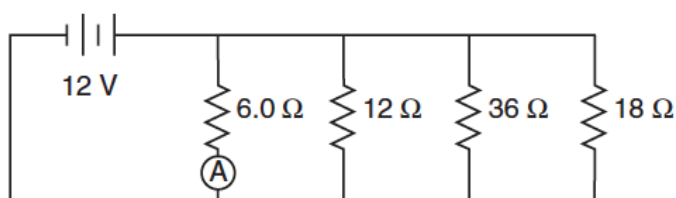
## HOMEWORK # 8 Circuit Analysis



Base your answers to questions 1 through 3 on the diagram below, which represents an electrical circuit consisting of four resistors and a 12-volt battery.



1. What is the current measured by ammeter A?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

2. What is the equivalent resistance of this circuit?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

3. How much power is dissipated in the 36-ohm resistor?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

4. Three resistors, 4 ohms, 6 ohms, and 8 ohms, are connected in parallel in an electric circuit. The equivalent resistance of the circuit is

a) less than 4 ohms

b) between 4 ohms and 8 ohms

c) between 10 ohms and 18 ohms

d) 18 ohms

5. A simple circuit consists of a 100-ohm resistor connected to a battery. A 25-ohm resistor is to be connected in the circuit. Determine the smallest equivalent resistance possible when both resistors are connected to the battery.


Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

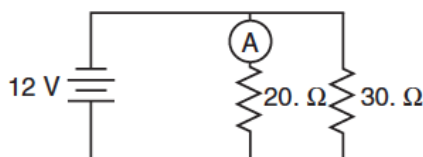**Base your answers to questions 6 through 8 on the information and diagram below.**

A 20-ohm resistor and a 30-ohm resistor are connected in parallel to a 12-volt battery as shown. An ammeter is connected as shown.



6. What is the equivalent resistance of the circuit?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

7. What is the current reading of the ammeter?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....


8. What is the power of the 30-ohm resistor?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

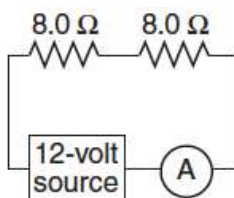9. The diagram below shows a circuit with two resistors.



What is the reading on ammeter A?





Equations:.....

Substitution of Values with Units:.....


Answers with Units:.....



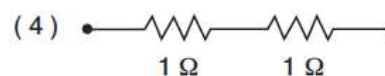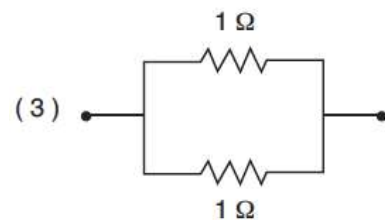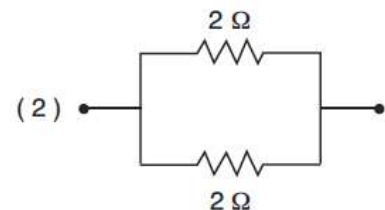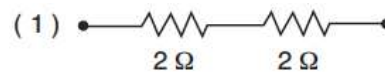10. Which combination of resistors has the smallest equivalent resistance?



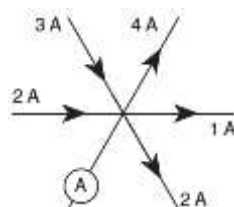11. The diagram below represents currents in a segment of an electric circuit.




What is the reading of ammeter A?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

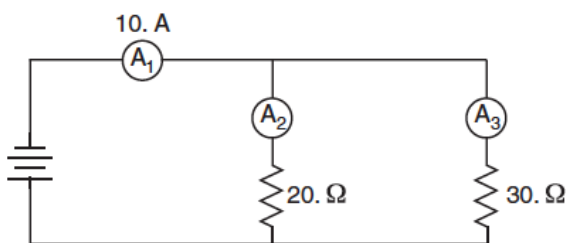12. In the circuit diagram shown below, ammeter  $A_1$  reads 10 amperes.




What is the reading of ammeter  $A_2$ ?

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

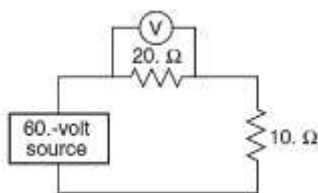13. In the circuit represented by the diagram below, what is the reading of voltmeter  $V$ ?




Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

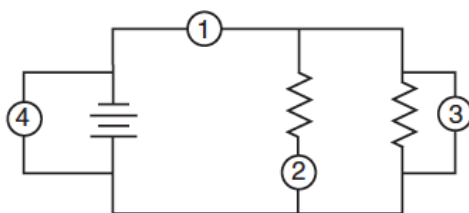14. In the electric circuit diagram below, possible locations of an ammeter and a voltmeter are indicated by circles 1, 2, 3, and 4.



Where should an ammeter be located to correctly measure the total current and where should a voltmeter be located to correctly measure the total voltage?

- a) ammeter at 1 and voltmeter at 4
- b) ammeter at 2 and voltmeter at 3

- c) ammeter at 3 and voltmeter at 4
- d) ammeter at 1 and voltmeter at 2



**Base your answers to questions 15 and 16 on the information below.**

A 15-ohm resistor and a 20-ohm resistor are connected in parallel with a 9-volt battery. A single ammeter is connected to measure the total current of the circuit.

15. Draw a diagram of this circuit using standard circuit schematic symbols.

**(Use an edge for drawing, e.g. ruler or metro card or ID card. Drawing without an edge will not be accepted.)**


16. Calculate the equivalent resistance of the circuit.

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

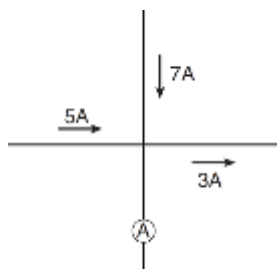17. The diagram below shows currents in a segment of an electric circuit.



What is the reading of ammeter A?


Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

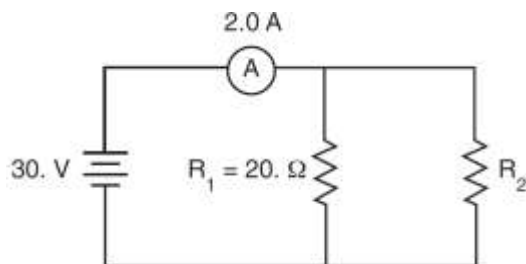**Base your answers to questions 18 and 19 on the information below.**

A 20-ohm resistor,  $R_1$ , and a resistor of unknown resistance,  $R_2$ , are connected in parallel to a 30-volt source, as shown in the circuit diagram below. An ammeter in the circuit reads 2.0 amperes.



18. Determine the equivalent resistance of the circuit.

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....

19. Calculate the resistance of resistor  $R_2$ .

Equations:.....

Substitution of Values with Units:.....

Answers with Units:.....